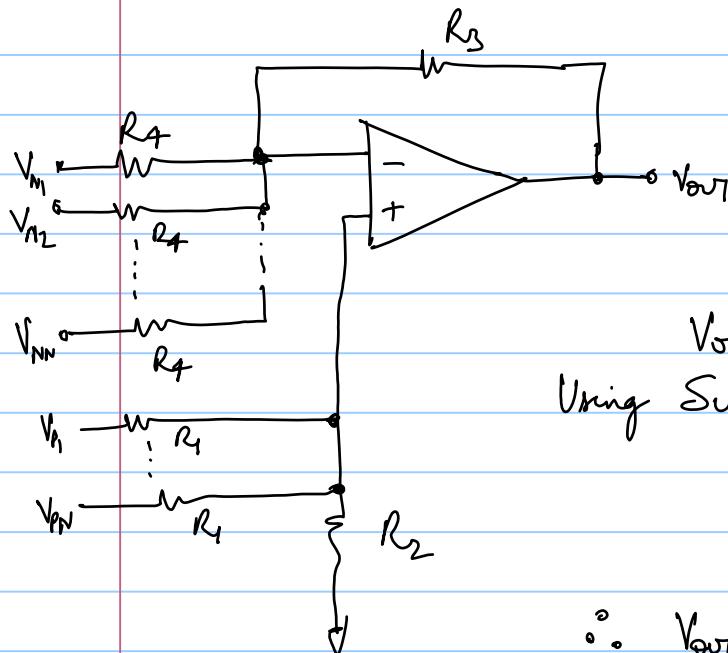


# N INPUT DIFFERENTIAL AMPLIFIER

Note Title

12/9/2010



If we want the transfer function:

$$V_{out} = K \left( \sum_i^N V_{pi} - \sum_i^N V_{Ni} \right)$$

Using Superposition we have:

$$\frac{V_{Ni}}{R_4} = -\frac{V_{out}}{R_3}$$

$$\therefore V_{out} = -\frac{R_3}{R_4} \sum_i^N V_{Ni}$$

Setting  $\frac{R_3}{R_4}$  gives us the part of the desired expression:

Using Superposition on  $V_{pi}$ 's we have:

$$\frac{V_{pi}}{\frac{R_2 \parallel \frac{R_1}{(N-1)}}{R_2 \parallel \frac{R_1}{(N-1)} + R_1} \left( \frac{NR_3}{R_4} + 1 \right)} = V_{out}$$

$$\therefore \text{we need } \frac{\frac{R_2 \parallel \frac{R_1}{(N-1)}}{R_2 \parallel \frac{R_1}{(N-1)} + R_1} \left( NK + 1 \right)}{K} = K$$

$$\Rightarrow \frac{\frac{R_1 R_2}{N-1} \left( \frac{R_1}{N-1} + R_2 \right)}{\left( \frac{R_1 + R_2}{N-1} \right) \left( \frac{R_1 R_2}{N-1} + R_1 \left( \frac{R_1}{N-1} + R_2 \right) \right)} (NK + 1) = K$$

$$\left( \frac{R_1 + R_2}{N-1} \right) \left( \frac{R_1 R_2}{N-1} + R_1 \left( \frac{R_1}{N-1} + R_2 \right) \right)$$

$$\Rightarrow \frac{R_1 R_2}{R_1 R_2 + R_1^2 + R_1 R_2 (N-1)} = (NK + 1) = K$$

$$\Rightarrow R_1 R_2 N K + R_1 R_2 = R_1 R_2 K + R_1^2 K + R_1 R_2 N K$$
$$\cancel{-R_1 R_2 K}$$

$$R_2 = R_1 K$$

or

$$\boxed{\frac{R_2}{R_1} = K}$$